

Multimeter

A multimeter is a versatile electronic measuring instrument used to measure voltage, current, and resistance. It is an essential tool for diagnosing electrical circuits.

What Does It Do?

- ❖ Measures voltage (in volts), current (in amperes), and resistance (in ohms).
- ❖ Helps in troubleshooting electrical and electronic devices.

How Does It Work?

- ❖ A multimeter uses probes to connect to the circuit.
- ❖ The black probe always connects to the common (COM) socket.
- ❖ The red probe is used in the V Ω socket for measuring voltage and resistance, and in a different socket when measuring current.
- ❖ To measure resistance, set the dial to the Ohm (Ω) symbol and connect the probes across the resistor.
- ❖ Resistance should be measured outside of a circuit, as current in a built circuit can bypass the resistor and give incorrect readings.

How to Control the Brightness of LEDs

LED brightness can be controlled using PWM (Pulse Width Modulation) instead of just lowering voltage or using a potentiometer.

1. Basic LED Dimming:

- ❖ A green LED typically runs at 3.2V.
- ❖ Reducing voltage below its forward voltage makes it dimmer, but this is inefficient and not practical for fixed voltage sources (like 5V or 12V).
- ❖ Using a potentiometer in series can dim LEDs but wastes power (as heat) and is not suitable for high-power LEDs.

2. PWM (Pulse Width Modulation):

- ❖ PWM switches the LED ON and OFF very fast.
- ❖ It uses full voltage (like 5V) but varies the duty cycle (ON-time percentage).
 - ✓ 100% duty cycle = fully bright.
 - ✓ 50% duty cycle = medium brightness.
 - ✓ 20% duty cycle = dim.
- ❖ Our eyes can't see the flicker; we only see the average brightness.

3. Generating PWM:

- ❖ With Arduino: Use `analogWrite(pin, value)` where:
 - ✓ `value` is from 0 (OFF) to 255 (fully ON).
 - ✓ A potentiometer can be used to adjust the value in real time.
- ❖ Without Arduino: Use a 555 timer IC to generate a PWM signal.
 - ✓ The duty cycle can be controlled with a potentiometer in the 555 circuit.
 - ✓ For higher power (like LED strips), use a MOSFET with the PWM signal connected to its gate.

Using and Programming the ATtiny85 with Arduino Uno

1. Efficient Microcontroller Use

- ❖ Instead of using a full ATmega328 (Arduino Uno), the ATtiny85 is a cost-effective and compact choice.
- ❖ It offers 5 I/O pins, 8KB flash memory, and is ideal for small projects like controlling WS2801 LED strips and handling a push button.

2. Programming the ATtiny85 with Arduino Uno

- ❖ Use the Arduino Uno as ISP (In-System Programmer).
- ❖ In Arduino IDE:
 - ✓ Upload `ArduinoISP` sketch from File > Examples > `ArduinoISP` to the Uno.

3. Arduino IDE Setup

- ❖ Use Arduino IDE 1.0.5 (newer versions may cause issues).
- ❖ Download ATtiny board support package from highlowtech.org.
- ❖ Extract and place the `attiny` folder into `arduino/hardware/arduino`.

4. Pin Mapping and Wiring

- ❖ ATtiny85 Pinout:
 - ✓ Pin 1: RESET
 - ✓ Pin 4: GND
 - ✓ Pin 8: VCC
 - ✓ I/O Pins: Pins 2 (PB3), 3 (PB4), 5 (PB0), 6 (PB1), 7 (PB2)
- ❖ Connect Arduino to ATtiny as follows:
 - ✓ Pin 13 → ATtiny pin 7
 - ✓ Pin 12 → ATtiny pin 6
 - ✓ Pin 11 → ATtiny pin 5
 - ✓ Pin 10 → ATtiny pin 1 (RESET)
 - ✓ 5V and GND accordingly
 - ✓ Add a 10μF capacitor between Uno RESET and GND.

5. Making a Programming Shield

- ❖ Create a custom shield using male headers and bridge wires on a small PCB.
- ❖ Solder IC socket and ensure correct traces for easy, reliable programming.

6. Bit-banged SPI Protocol

- ❖ ATtiny85 lacks hardware SPI support.
- ❖ Use bit-banged SPI (software emulated SPI), e.g., from SparkFun libraries, to control devices like WS2801 LED strips.

Bluetooth Arduino LED Control

How to use a Bluetooth module (HC-05) to control an RGB LED with an Arduino Nano via a smartphone using the S2 Terminal app.

1. Bluetooth Module:

- ❖ HC-05 (4-pin module). Be careful—some units can arrive faulty or be damaged by incorrect wiring.

2. Logic Level Difference:

- ❖ Arduino uses 5V logic; HC-05 uses 3.3V. Use a voltage divider (2k Ω and 4.7k Ω resistors) to safely connect Arduino TX to module RX.

3. Wiring:

- ❖ TX (Arduino) \rightarrow Voltage Divider \rightarrow RX (Bluetooth)
- ❖ RX (Arduino) \leftarrow TX (Bluetooth)
- ❖ RGB LED: Common anode; cathodes with $\sim 460\Omega$ resistors to pins 8, 9, 10

4. App Used: S2 Terminal (Android) :

- ❖ send ASCII code words like `red`, `green`, `blue` to control LED.

5. Arduino Code:

- ❖ Modify the code words and LED control logic as desired.

6. Upload Tip: Disconnect TX/RX:

- ❖ wires before uploading code to avoid interference.

7. Pairing:

- ❖ Device name usually HC-05, default code `1234` or `0000`.

Result:

Sending commands from our phone changes the LED color and receives confirmation via serial.

Perfect for beginners exploring Bluetooth + Arduino projects.

Efficient Control of LED Matrices and Cubes Using Multiplexing and TLC5940

1. Problem: Limited I/O Pins for Many LEDs

- ❖ Large LED setups like a 4x4x4 RGB cube (192 LEDs) or a 10x5 matrix (50 LEDs) require more microcontroller pins than available.
- ❖ Even Arduino Mega's 54 I/O pins are insufficient for direct control.

2. Solution: Multiplexing

- ❖ Connect all LED cathodes (negative pins) in each column together.
- ❖ Connect all LED anodes (positive pins) in each row together.
- ❖ Light up LEDs row-by-row very fast, so the eye sees a steady image.
- ❖ Only one row is powered at a time, preventing electrical conflicts.

3. Hardware Components Used

- ❖ Arduino Nano as the microcontroller.
- ❖ TLC5940 LED driver for controlling LED columns and providing constant current.
- ❖ P-Channel MOSFETs (F9540N) as switches for each anode row to handle high current.
- ❖ Resistors: $5 \times 1\text{K}\Omega$ pull-ups for MOSFET gates, $1 \times 2\text{K}\Omega$ for setting TLC5940 current to 20mA per LED.

4. Wiring Overview

- ❖ Rows (anodes) connected through MOSFETs to Arduino pins (e.g., pins 4-8).
- ❖ Columns (cathodes) connected to TLC5940 outputs.
- ❖ MOSFET gates connected to Arduino pins with pull-up resistors to 5V.
- ❖ 2K resistor sets the current on TLC5940's reference pin.

5. Programming and Control

- ❖ Use a pre-made TLC5940 Arduino library to simplify coding.
- ❖ Code multiplexes rows, switching them quickly.
- ❖ Example code shows effects like a moving sine wave and scrolling text.
- ❖ Adjusting row on-time affects visible flicker and brightness.

6. Benefits and Applications

- ❖ Enables control of many LEDs with minimal microcontroller pins.
- ❖ Ideal for complex displays such as LED matrices or RGB LED cubes.
- ❖ Multiplexing with constant current drivers ensures stable, bright, and efficient LED control.

Building a Standalone Arduino with ATmega328P

1. Overview

- ❖ Move from breadboard to a compact gadget by embedding the ATmega328P microcontroller.

2. Required Components

- ❖ ATmega328P
- ❖ 16 MHz crystal + two 22 pF capacitors
- ❖ 10 k Ω resistor on reset pin
- ❖ Power: pins 7, 20, 21 \rightarrow 5V; pins 8, 22 \rightarrow Ground

3. Clock Options

- ❖ Use external 16 MHz crystal (default)
- ❖ Or 8 MHz internal oscillator with a different bootloader

4. Limitations vs Arduino Board

- ❖ No reset button, USB-to-serial, or power protection.

5. Programming Methods

- ❖ Remove chip, program on Arduino board
- ❖ Use Arduino as USB-to-serial adapter (connect TX/RX/reset)
- ❖ Use USB-to-serial converter chip (e.g., FTDI)

6. Final Tips

- ❖ Test on breadboard first and add headers for easy reprogramming.

Using 7-Segment Displays with and without Arduino

1. Introduction to 7-Segment Displays

- ❖ Old-school but useful for simple numeric outputs (clocks, sensors, power meters).
- ❖ Common types: single digit, two-digit displays.
- ❖ Always check the datasheet for pin configuration.
- ❖ Example: LTS546A, common anode with 7 bars (A-G) + decimal point (DP).

2. Displaying Numbers Without a Microcontroller

- ❖ Use a BCD to 7-segment driver IC like SN74LS247 (active low for common anode).
- ❖ Connect bars through 220Ω resistors to limit current.
- ❖ Control inputs (A, B, C, D) select which number to display.
- ❖ Combine with a 4-bit binary counter (SN74290) to cycle through numbers.
- ❖ Clock input can be triggered by buttons or sensors.

3. Handling Multiple Digits

- ❖ Two-digit displays have two common anodes; multiplexing is required.
- ❖ Multiplexing reduces pin usage by switching digits rapidly.
- ❖ Example: use 8 pins for segments + 4 pins for common anodes.

4. Using Dedicated Driver IC (SLA1064)

- ❖ Controls up to 4 digits by multiplexing 2 at a time; multiple ICs can chain up to 16 digits.
- ❖ Uses I²C communication (supported by Arduino).
- ❖ Requires pull-up resistors, speed-setting capacitor, and transistors for multiplexing.
- ❖ Easier to handle multiple digits with less Arduino pin usage and processing power.
- ❖ Use existing libraries for simpler coding.

5. Summary

- ❖ 7-segment displays are still great for simple numeric projects. You can drive them with logic ICs or microcontrollers using direct pins or I²C drivers, depending on complexity. Multiplexing is key for multi-digit displays.

Mastering LEDs: From Simple Circuits to Advanced Driving Techniques

1. Basic LED Setup

- ❖ Key Specs: Forward voltage (e.g. 3.2V) and current (20mA).
- ❖ Power Source Example: 9V battery.
- ❖ Why Resistors Matter: Without one, LEDs burn out instantly.
- ❖ Resistor Calculation:
 - ✓ Use Ohm's Law:
 - Voltage drop = Power source – LED voltage
 - Resistance = Voltage drop / Current
 - ✓ Example: $(9V - 3.2V) / 0.02A = 290\Omega$
 - ✓ Choose higher resistance if exact value isn't available.

2. Power & Efficiency

- ❖ Resistor power rating = Voltage drop \times Current.
- ❖ Ensure it's below the resistor's rated wattage (e.g. 0.25W).
- ❖ Series LED setup saves power vs parallel.

3. Advanced Considerations

- ❖ Forward Voltage Variability: Real-world LEDs may differ.
- ❖ Tiny Voltage Changes = Big Current Changes
 - ✓ Always use a resistor, even if forward voltage matches power source.
- ❖ Don't Parallel LEDs with One Resistor:
 - ✓ Different forward voltages cause uneven current draw.
 - ✓ Some LEDs overheat and die sooner.

4. Better LED Driving Methods

- ❖ Constant Current Mode > Constant Voltage Mode
 - ✓ All LEDs want same current, not exact voltage.
- ❖ Constant Current Circuit:
 - ✓ Use LM317 and a resistor.
 - ✓ Efficient alternatives: ICs like TLC5940 (covered in future videos).

Understanding Diodes: The One-Way Valve of Electronics

1. Diode

- ❖ A diode allows current to flow in only one direction: from anode to cathode.
- ❖ Commonly used in both DC and AC circuits for protection and rectification.

2. Diode in DC Circuits (Polarity Protection)

- ❖ Prevents damage when power is connected with wrong polarity.
- ❖ Example: In a 5V circuit, a diode blocks reverse current if polarity is flipped.
- ❖ Voltage Drop: Diodes are not perfect. A 1N4007 diode drops $\sim 0.65V$ under load, so the output may be around 4.35V instead of 5V.
- ❖ Power Loss: This drop causes some heat and power loss, especially under high current loads.

3. Diode in AC Circuits (Rectification)

- ❖ Used to convert AC to DC.
- ❖ A single diode produces half-wave rectification (removes negative cycle).
- ❖ Problem: Output is bumpy and inconsistent.

4. Bridge Rectifier (Full-Wave Rectification)

- ❖ Uses 4 diodes in a specific arrangement.
- ❖ Converts both halves of the AC signal into a unidirectional (positive) flow.
- ❖ Smoother and more efficient than half-wave.

5. Capacitor for Smoothing DC

- ❖ Adding a capacitor after the diode or bridge rectifier smooths out the DC signal.
- ❖ Under load, the capacitor discharges between waves, making the output bumpy again if not sized properly.

6. Real-World Usage

- ❖ Diodes are found in all power supplies, from old linear ones to modern switching types.
- ❖ Also found in consumer electronics (e.g., SMD diodes in microcontrollers).

Understanding DAC (Digital to Analog Converter): From Code to Sound

1. DAC

- ❖ A DAC (Digital to Analog Converter) transforms digital signals (1s and 0s) into analog voltages (like sine waves).
- ❖ Useful in audio devices, signal generation, and analog control.

2. Digital vs Analog Signals

- ❖ Digital: Only two states (HIGH/LOW or 1/0).
- ❖ Analog: Smooth continuous signals (sine, triangle, ramp, etc.).

3. Resistor Ladder DAC (R-2R Method)

- ❖ Made using two resistor values (e.g., $10\text{k}\Omega$ and $20\text{k}\Omega$).
- ❖ Digital pins from microcontrollers (like Arduino Nano) send binary values.
- ❖ Output voltage corresponds to the binary number applied (e.g., binary 128 gives $\sim 2.3\text{V}$ if max is 4.8V).

4. Signal Generation Using DAC

- ❖ Ramp Function: Gradually increase values from 0 to 255, then back to 0.
- ❖ Triangle Wave: Rise to 255, fall to 0, and repeat.
- ❖ Sine Wave: Send sine-calculated values; produces sound-like waveform.

5. Output Stability with Op-Amps

- ❖ Directly connecting a speaker to a resistor ladder distorts the output.
- ❖ Use an Op-Amp in voltage follower mode to maintain output stability without amplification.

6. Arduino's `analogWrite()` and PWM

- ❖ `analogWrite()` doesn't give true analog output—it gives a PWM (Pulse Width Modulated) signal.
- ❖ Needs a low-pass filter (resistor + capacitor) to smooth the output into analog.

7. Ready-Made DAC ICs

- ❖ DAC0800: An 8-bit DAC chip.
- ❖ PCF8591: Budget 8-bit DAC with I²C interface.
- ❖ MCP4725: High-quality 12-bit DAC via I²C, precise and compact.

Sending SMS with TC35 GSM Module and Arduino UNO

1. Overview of the TC35 GSM Module

- ❖ Price: Around \$23 (cheaper options available).
- ❖ Manufacturer: Module by Siemens, board likely from a Chinese brand.
- ❖ Requirement: Needs a SIM card (prepaid recommended).
- ❖ Initial Setup: Remove SIM lock using a smartphone before inserting into the module.

2. Powering the Module

- ❖ Power Input Options:
 - ✓ DC Jack
 - ✓ VCC & GND pins (recommended: 5V)
- ❖ Important Note:
 - ✓ Avoid using over 6V unless MAX232 IC is removed (as it's directly powered and has a 6V max limit).
 - ✓ Without RS232 use, the module uses less power (6mA standby).

3. Starting the Module

- ❖ Manual Start: Press button on board.
- ❖ Automatic Start:
 - ✓ Solder jumper wire to the right side of the button (connect to pin 10 on Arduino).
 - ✓ Pulling pin LOW starts the module.
 - ✓ Power usage in this state: ~13mA.

4. Communication with the Module

- ❖ Using FTDI Adapter:
 - ✓ TX → TXD0
 - ✓ RX → RXD0 (Labeling is reversed on this board)
 - ✓ GND → GND
- ❖ Voltage Compatibility:
 - ✓ Module uses 3.3V logic, but works fine with 5V FTDI or Arduino signals.

5. Using AT Commands

- ❖ Open Arduino Serial Monitor (9600 baud, carriage return selected).
- ❖ Examples:

- ✓ AT → should return OK
- ✓ Check signal strength, operator name, etc.

6. Sending an SMS via Arduino

- ❖ Circuit: Simple wiring (TX, RX, GND, power, and button trigger pin).
- ❖ Code:
 - ✓ Provided Arduino sketch sends SMS.
 - ✓ Input text via serial monitor.
 - ✓ End the message with a dot (.) to send.
- ❖ Phone Number Format:
 - ✓ Country code (e.g., 49 for Germany), followed by number (without leading 0).

7. Applications & Future Use

- ❖ Code can be modified for custom projects.
- ❖ Future use example: SMS-based alarm system.

Understanding Inductors (Coils) – Basics and Applications in DC Circuits

1. Inductors

- ❖ Inductors (or coils) are passive electronic components.
- ❖ Found in motors, transformers, relays, and many other devices.
- ❖ Their function is tied to magnetic fields generated by current flow.

2. Magnetic Field and Induction Basics

- ❖ When current flows through a wire, it creates a magnetic field.
- ❖ More current = stronger field.
- ❖ Wrapping the wire into a coil increases magnetic strength.
- ❖ Adding a ferromagnetic core (like iron) greatly boosts the magnetic field.
- ❖ This creates an electromagnet, which is the working principle behind relays and motors.

3. Inductance

- ❖ Inductance (measured in Henrys) defines how much magnetic energy a coil can store.
- ❖ Depends on:
 - ✓ Number of turns in the coil.
 - ✓ Coil dimensions.
 - ✓ Core material.
- ❖ Can be measured using an RLC meter.

4. Coil Behavior in DC Circuits

- ❖ In DC, voltage only turns on or off.
- ❖ Current in a coil does not change instantly.
- ❖ This is due to Lenz's Law:
 - ✓ Coil opposes change in current flow.
 - ✓ When current starts, coil slows it down.
 - ✓ When current stops, coil pushes back with its stored magnetic energy.

5. Applications of Inductors

- ❖ Energy Storage:
 - ✓ Used in boost converters to raise voltage (e.g., $3.7V \rightarrow 5V$).

❖ Motor Control:

- ✓ Coils in motors cause voltage spikes when switched.
- ✓ A flyback diode is used to protect circuits from these spikes.

❖ Power Supplies:

- ✓ Coils help maintain constant voltage output in switching power supplies.

6. Key Concepts to Remember

❖ Energy stored in a coil:

$$E = \frac{1}{2}LI^2$$

- ❖ Coils resist changes in current, making them useful in filtering, energy storage, and surge protection.

Understanding Inductor Basics and Inductive Reactance

1. LED Circuit Behavior with and without an Inductor

- ❖ A simple LED connected directly to a 230V–15V RMS transformer dies quickly.
- ❖ When a 1.5H inductor (coil) is added in series, the LED lights up safely.
- ❖ Replacing the coil with a resistor of equal resistance (~33 ohms) still burns the LED.

2. Inductive Reactance Explained

- ❖ Reactance is a frequency-dependent resistance due to inductance.
- ❖ Formula: $X_L = 2\pi f L$
- ❖ Power oscillates between the source and the coil, leading to reactive power, which stresses the power grid.

3. Effect of Frequency on Reactance

- ❖ Increasing the frequency increases inductive reactance, reducing current and dimming the LED.
- ❖ Demonstrates the time-limited current flow at high frequencies.

4. Practical Applications of Reactance

- ❖ Inductors can be used to create frequency filters:
 - ✓ High-pass filter: Allows frequencies above a threshold.
 - ✓ Low-pass filter: Allows frequencies below a threshold.
- ❖ Demonstrated with LTSpice simulation and MOSFET circuit for detecting high-frequency signals.

5. Phase Shift in Inductive Circuits

- ❖ Voltage and current waveforms are out of phase in inductive loads.
- ❖ Phase shift indicates the level of inductance.
- ❖ Example: A microwave motor shows a 36° phase shift, confirming it's an inductive load.

6. Measuring Inductance Affordably

- ❖ A \$20 transistor tester from Amazon/eBay is a budget-friendly tool for measuring inductance, resistance, capacitance, and transistor gain.
- ❖ Based on a reliable German microcontroller project.

Exploring Capacitors: Function, Construction & Circuit Applications

1. Capacitor

- ❖ A capacitor stores electrical energy in the form of an electrostatic field between two conductive plates.
- ❖ Created using two metal plates separated by a small gap or insulating dielectric material.
- ❖ When voltage is applied, electrons accumulate on one plate, creating a temporary electric field.

2. Building and Improving a Capacitor

- ❖ Capacitance increases by:
 - ✓ Enlarging plate surface area.
 - ✓ Reducing the distance between plates.
 - ✓ Inserting a dielectric like distilled water to align dipoles and enhance the field.
- ❖ Example: Homemade capacitor reached up to 2.5 microfarads using this method.

3. Real-World Capacitors

- ❖ Electrolytic capacitors use tightly packed metal films and dielectric materials.
- ❖ Important considerations:
 - ✓ Do not exceed voltage rating to avoid breakdown.
 - ✓ Avoid reverse polarity, especially with electrolytic types.

4. Capacitors in Circuits

- ❖ DC Behavior:
 - ✓ Voltage across a capacitor cannot change instantly.
 - ✓ Used for voltage smoothing, decoupling ICs, and timing circuits (e.g., with 555 timers).
- ❖ AC Behavior:
 - ✓ Introduce capacitive reactance $X_C = \frac{1}{2\pi fC}$.
 - ✓ Higher frequency or capacitance = lower reactance (more current flows).
 - ✓ Capacitors act as frequency-based resistors.

5. Applications of Capacitors

- ❖ Used in RC filters:
 - ✓ High-pass and low-pass filters for audio or signal processing.
 - ✓ Preferred over coils due to cost and compact size.
- ❖ Power factor correction:
 - ✓ Inductive loads like motors create phase shifts, causing reactive power.
 - ✓ Adding capacitors in parallel offsets this and relieves the power grid.

Understanding Temperature Measurement: From Thermistors to DIY Thermometers

1. Importance of Accurate Temperature Measurement

- ❖ Crucial for applications like 3D printing, electronics, and industrial systems.
- ❖ Requires selecting suitable sensors for accuracy, range, and responsiveness.

2. Common Temperature Sensors

- ❖ NTC Thermistors (Negative Temperature Coefficient)
 - ✓ Resistance decreases with increasing temperature.
 - ✓ Available in various values (1K, 10K, etc.).
 - ✓ Offer high resolution, but are non-linear and less precise.
 - ✓ Limited to $\sim 150^{\circ}\text{C}$.
- ❖ PT100 RTD (Resistance Temperature Detector)
 - ✓ Resistance increases with temperature.
 - ✓ More linear and accurate than thermistors.
 - ✓ Can measure up to 850°C .
 - ✓ Requires constant low current (e.g., 1mA) for accurate reading.

3. Measuring Techniques

- ❖ Basic Measurement (Ohm's Law)
 - ✓ Apply constant current and measure voltage to calculate resistance.
 - ✓ Issues: low voltage range and offset at 0°C .
- ❖ Offset Correction Methods
 - ✓ Voltage Divider & Differential Op-Amp: Removes voltage offset.
 - ✓ Wheatstone Bridge: Balances voltages for more accurate readings.
 - ✓ Both require precise resistor values and amplification.

4. Simplified Alternative: Temperature Transmitter

- ❖ Converts PT100 signal to standard 4–20 mA current loop.
- ❖ Inexpensive ($\sim \$5$) and offers 0.2% accuracy.
- ❖ Easy to integrate with microcontrollers using a resistor and analog input.
- ❖ Supports 2-wire and 3-wire configurations (minimizes wire resistance errors).

5. DIY Thermometer Example

- ❖ Components: PT100, transmitter, 16x2 LCD, microcontroller.
- ❖ Code reads analog input, maps voltage to temperature, and displays output.
- ❖ Worked reliably for both sub-zero and positive temperatures.

6. IC-Based Temperature Sensors

- ❖ LM35: Outputs 0–1.5V linearly for 2–150°C, $\pm 0.5^\circ\text{C}$ accuracy.
- ❖ DS18B20: Digital output via one-wire interface, $\pm 0.5^\circ\text{C}$ accuracy.
- ❖ Easier to use but generally slower due to thermal inertia.

Essential Applications of Resistors in Electronics

1. Basic LED Protection

- ❖ Resistors are crucial for limiting current in simple circuits like an LED with a power source.
- ❖ Without a resistor, LEDs may burn out instantly.
- ❖ Using Ohm's Law ($V = IR$), resistance is calculated to protect components (e.g., $\sim 524\Omega$ for a 5mm LED with 10.48V supply and 20mA current).
- ❖ Power resistors may be required for higher voltages to handle more heat dissipation.

2. Voltage Division

- ❖ Resistors can divide voltages for logic level conversion (e.g., 5V Arduino to 3.3V ESP8266).
- ❖ Useful when interfacing different microcontrollers or modules.

3. Adjustable Voltage with Potentiometers

- ❖ Potentiometers are variable resistors with movable contact for adjusting resistance.
- ❖ Commonly used to tune analog inputs or set voltages dynamically.

4. Pull-up and Pull-down Resistors

- ❖ Prevent floating input states in microcontrollers:
 - ✓ Pull-down resistor connects input to ground (logic 0).
 - ✓ Pull-up resistor connects input to V_{cc} (logic 1).
- ❖ Essential for stable input reading from buttons or switches.

5. Current Sensing

- ❖ Low-value resistors used to measure current by detecting voltage drop.
- ❖ Paired with differential amplifiers to monitor current flow.
- ❖ Enables building constant current sources or electronic loads.

6. Resistors as Fuses

- ❖ Deliberately choosing resistors to burn out at high currents protects sensitive circuits.
- ❖ Acts as a simple fuse substitute.

7. AC Behavior and Parasitic Effects

- ❖ Ideal resistors behave the same in AC and DC, but at higher frequencies, parasitic capacitance/inductance becomes significant.
- ❖ These parasitic effects alter impedance and can impact circuit performance.
- ❖ Important to consider in high-frequency or precision circuits.

Understanding Oscillators: The Heartbeat of Electronic Timing

1. Oscillators

- ❖ Oscillators are electronic circuits that generate periodic signals (square, sine, triangle waves).
- ❖ They are crucial in timing systems, clocks, microcontrollers, displays, and wireless communication.

2. RC-Based Relaxation Oscillators

- ❖ A classic astable multivibrator uses resistors and capacitors (RC) with transistors to create a square wave.
- ❖ The oscillation is controlled by charging/discharging capacitors, switching transistors alternately.
- ❖ Changing resistor/capacitor values alters the frequency.

3. 555 Timer Oscillator

- ❖ Popular and simple IC for creating square waveforms.
- ❖ Works by charging a capacitor between 33% and 66% of the supply voltage.
- ❖ Easy to build with a capacitor, resistor, and potentiometer for adjustable frequency output.

4. LC Tank Circuits (Resonators)

- ❖ Combine inductors (L) and capacitors (C) to create sine wave oscillations.
- ❖ The capacitor's energy converts into magnetic energy in the inductor and back again, creating resonance.
- ❖ The resonant frequency is where inductive and capacitive reactance cancel out.

5. Sustaining Oscillations with Amplifiers

- ❖ LC circuits lose energy due to resistance.
- ❖ Using an amplifier (e.g., an NPN transistor), you can reintroduce energy into the tank circuit to maintain oscillations.
- ❖ Ideal for high-frequency generation.

6. Crystal Oscillators

- ❖ Use piezoelectric crystals to generate extremely stable oscillations.
- ❖ Often found near microcontrollers (e.g., 16 MHz crystals) to define processing speed.
- ❖ They behave like high-Q LC circuits, with better frequency stability.

Understanding Brushless DC Motors and ESCs

1. Introduction to Brushless Motors

- ❖ Brushless DC motors (BLDC) are widely used in electric skateboards, drones, and electronic devices like DVD drives.
- ❖ They operate alongside an Electronic Speed Controller (ESC) to manage speed and rotation.

2. Basic Working Principle (Using Brushed DC Motors)

- ❖ In brushed DC motors, current flows through carbon brushes and a commutator to energize coils.
- ❖ Coils interact with permanent magnets, generating rotational motion.
- ❖ The commutator automatically switches polarity, ensuring continuous rotation.

3. Brushless Motor Construction

- ❖ Rotor: Contains permanent magnets (often 4 or more).
- ❖ Stator: Contains multiple coils (e.g., 12), arranged in a star connection.
- ❖ Instead of a mechanical commutator, BLDC motors use electronic switching via the ESC.

4. Role of the ESC (Electronic Speed Controller)

- ❖ The ESC controls the timing and energizing of coil pairs in a 6-step cycle.
- ❖ It uses PWM (Pulse Width Modulation) and an array of MOSFETs to switch between high, low, and floating states.
- ❖ Higher frequency switching leads to higher RPM.

5. Factors Affecting Motor Performance

- ❖ Number of coils/magnets: More coils and magnets = lower RPM, higher torque.
- ❖ Outrunner motors: Preferred for applications needing high torque.
- ❖ ESC design: Number of MOSFETs affects how much current it can handle.
- ❖ Load and voltage: Heavier loads draw more current; voltage impacts RPM via increased switching frequency.

6. KV Rating Explained

- ❖ KV = RPM per volt (e.g., a 520 KV motor gives 520 RPM per volt).
- ❖ Higher KV = higher RPM, lower torque.
- ❖ RPM also depends on motor characteristics and ESC frequency, not just voltage alone.

Understanding I²C (Inter-Integrated Circuit) Communication Protocol

1. Introduction to I²C

- ❖ I²C (also called Two-Wire Interface) is a synchronous serial communication protocol.
- ❖ It allows one master (e.g., Arduino Nano) to communicate with up to 112 slave devices using only two wires:
 - ✓ SDA (Serial Data)
 - ✓ SCL (Serial Clock)

2. Basic Circuit Setup

- ❖ Example device: TEA5767 FM Radio IC
- ❖ Key connections:
 - ✓ SDA to A4, SCL to A5 of Arduino
 - ✓ Two 10kΩ pull-up resistors for stable voltage states
- ❖ Power, ground, antenna, and audio out were connected accordingly

3. Communication Basics

- ❖ Start Condition: Data line goes low while clock is high (handled by Arduino's `Wire` library)
- ❖ Device Address: 7-bit value from the datasheet, followed by R/W bit (0 = write, 1 = read)
- ❖ ACK Bit: Sent by the slave to confirm readiness
- ❖ Data Bytes: 5 bytes sent to define the desired operation (e.g., tuning frequency)

4. Tuning the FM Frequency

- ❖ Example frequency: 95.6 MHz
- ❖ PLL value calculated using a datasheet formula
- ❖ PLL and control bytes converted to hexadecimal
- ❖ Data sent through Arduino code using the `Wire` library functions

5. Testing and Output

- ❖ Initial audio was low; adding an amplifier improved clarity
- ❖ Oscilloscope used to analyze the I²C signals and confirm proper communication
- ❖ A read function was implemented to receive station data and display it on the Serial Monitor

6. Scalability and Other Protocols

- ❖ Multiple slave devices can share the same I²C bus
- ❖ Other communication protocols include SPI, One-Wire, etc., for future exploration

Understanding Thyristors and Building a Phase Angle Control Circuit

1. Introduction to Thyristors

- ❖ Unlike diodes (2 semiconductor layers), thyristors have 4 layers and an extra gate terminal.
- ❖ Thyristors act as controllable diodes that can be turned on by a gate signal.
- ❖ Example: TYN 604 thyristor, rated for 600V and 4A.

2. Basic Operation and Characteristics

- ❖ Applying a positive voltage to the gate triggers conduction; the load (e.g., LED) lights up.
- ❖ Thyristor remains on (latched) even after gate voltage is removed, as long as current > holding current (~30mA).
- ❖ To turn off, current must drop below holding current or be interrupted (e.g., with MOSFET).
- ❖ Turn-off time (~37 microseconds) defines how quickly the thyristor stops conducting after current interruption.

3. Handling Larger Loads and Heat Dissipation

- ❖ Larger loads (e.g., 2A light bulb) cause heating in the thyristor due to voltage drop and power loss.
- ❖ Heat sinks are needed to manage thermal dissipation.

4. AC Voltage Challenges and TRIACs

- ❖ When used with AC, thyristors turn off at zero-crossing (natural zero points in AC waveform).
- ❖ Half-wave control limits power and can't block negative half cycles.
- ❖ Solution: Use two thyristors in inverse parallel or a TRIAC (a pre-made bidirectional thyristor).

5. Phase Angle Control Circuit with Arduino

- ❖ Uses:
 - ✓ Full bridge rectifier and optocoupler to detect zero-cross points of AC.
 - ✓ Arduino Nano uses zero-cross detection on an interrupt pin.
 - ✓ Delay controlled by potentiometer determines when to trigger TRIAC.
 - ✓ TRIAC activation controls the power delivered to the load (e.g., light bulb).

6. Applications and Considerations

- ❖ Used for controlling power in AC appliances (lights, motor speed).
- ❖ Downsides include reduced power factor due to non-sinusoidal current.
- ❖ Suitable for testing and experimental purposes.

Understanding Operational Amplifiers (Op-Amps) and Their Practical Applications

1. Op-Amp

- ❖ An Op-Amp (Operational Amplifier) is a triangle-shaped analog component used in both analog and digital circuits.
- ❖ Common ICs: LM358 (dual op-amp) and others in 8 or 14-pin DIP packages.
- ❖ Has inverting (-) and non-inverting (+) inputs, and an output.
- ❖ Needs a power supply: e.g., 0V (GND) and +12V.

2. Key Concepts & Rules

- ❖ Golden Rule 1: Op-amp output adjusts to keep voltage difference between its inputs at zero volts (in closed-loop).
- ❖ Golden Rule 2: Op-amp inputs draw no current (ideal case).
- ❖ Golden Rule 3: Without feedback, op-amp works as a comparator—output saturates high or low depending on input comparison.

3. Non-Inverting Amplifier

- ❖ Input applied to non-inverting pin.
- ❖ Gain determined by resistor values:
 $\text{Gain} = 1 + (R2 / R1)$
- ❖ Used to amplify small signals, like sensor voltages or microphone outputs.

4. Dealing with AC Signals

- ❖ AC signals may only get partially amplified due to single supply limitation.
- ❖ Solutions:
 - ✓ Use dual supply ($\pm 12\text{V}$).
 - ✓ Add a DC offset to allow full waveform swing.
- ❖ Watch out for output swing limits (e.g., 10.8V max even if 12V is supplied).

5. Inverting Amplifier

- ❖ Input connected via resistor to inverting pin, non-inverting input grounded or biased.
- ❖ Gain formula:
 $\text{Gain} = - (R2 / R1)$
- ❖ Good for AC signal amplification with a DC offset, avoiding DC amplification issues.

6. Comparators

- ❖ When used without feedback, op-amps compare input voltages and saturate output.
- ❖ Dedicated comparator ICs are faster and better for such tasks.

7. Applications

- ❖ Op-Amps are versatile and can be used to build:
 - ✓ Voltage followers (buffer)
 - ✓ Summing amplifiers
 - ✓ Difference amplifiers
 - ✓ Schmitt triggers
 - ✓ Integrators and differentiators
 - ✓ Constant current sources
- ❖ Important for analog signal processing.